

6. An energy-saving system is installed in a new office block. If the natural light level in an office is high enough, the lights turn off automatically. The control circuit is shown in Figure Q6.

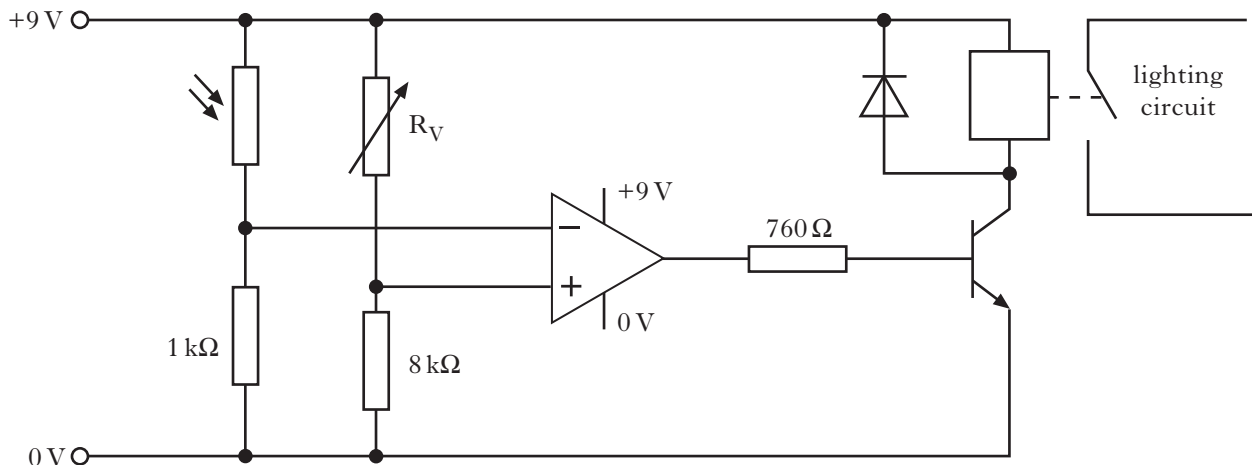


Figure Q6

- (a) Calculate the value of R_V so that the light circuit switches off at 650 lux. 2
- (b) Calculate the base current when the op-amp output is high. 2
- The resistance of the relay is $15\ \Omega$.
- (c) (i) Calculate the collector current when the transistor saturates. 1
- (ii) Calculate the minimum current gain of the transistor. 1
- (iii) State which of the transistors shown in the table below is most suitable for this circuit. 1
- (7)**

Device	$V_{CE(max)}$ (V)	$I_c(max)$ mA	h_{FE}
2N3704	30	600	100
BC108	25	200	100
BC142	60	1000	20
BC182	50	100	120
BC548b	30	100	220
BFY51	30	1000	40

[Turn over

9. (continued)

When the ignition is turned on the system performs a check of the sensors. If a fault is detected a warning lamp is illuminated. The op-amp-based system shown in Figure Q9(c) performs this check.

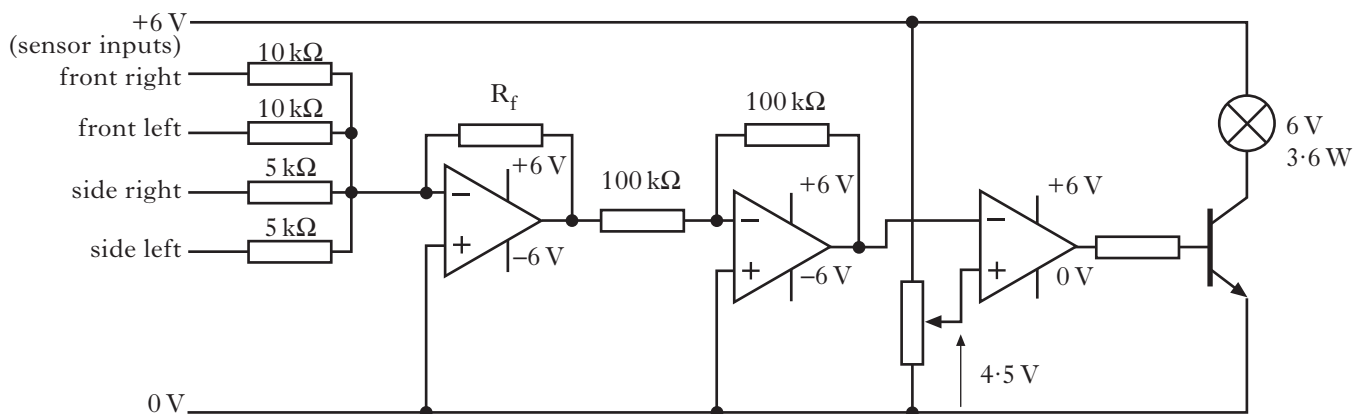


Figure Q9(c)

When the car is stationary a front sensor should have an output voltage of 1.2 V and a side sensor should have an output of 0.6 V.

- (e) Calculate an appropriate value for R_f so that the warning lamp will light if any of the sensors produce a test voltage output below the correct value. 2

A bipolar transistor-based driver circuit controls the lamp.

When a fault exists, the base current is 15.5 mA and the voltage across the lamp is 6 V.

- (f) Calculate the minimum current gain for the driver circuit. 1
- (20)**